# Diodes in Relay Protection



## Overview

Do Relays Have Diodes?

| Flyback Diodes Protect RelayYes, relays can have diodes. Specifically, many relays include a flyback diode, also known as a freewh.

## Key Takeaways

Diodes are used in relay circuits primarily to suppress back EMF and protect control electronics from voltage spikes generated when the relay coil is de-energized.

### Function of Diodes in Relay Circuits

When a relay coil is energized, it creates a magnetic field that operates the relay contacts. When the coil is de-energized, this magnetic field collapses, generating a high-voltage spike in the opposite direction, known as back EMF. This spike can damage sensitive components such as transistors, microcontrollers, or PLC inputs.

A diode placed across the relay coil, in reverse bias relative to the supply voltage, provides a safe path for this energy, allowing it to circulate through the coil and diode until it dissipates, preventing damage to the driving circuit (flyback diode).

### Types of Diodes Used

Flyback Diode (Standard Rectifier Diode): The most common type, such as 1N4007, used to suppress back EMF in DC relay circuits. Avalanche or Zener Diodes: Used for polarity-insensitive protection and to handle higher voltage surges. A double Zener diode can protect both the relay coil and the control electronics from surges in either direction.

© 2026 CJC FIBRE CONSULTANTS - All rights reserved

Polarization Diode: Ensures that no current flows if the relay is connected with reversed polarity, preventing damage.

### Installation Considerations

The diode should be connected in parallel with the relay coil, with the cathode to the positive supply and anode to the negative side, so it does not conduct during normal operation. It is recommended to place the diode as close to the relay coil as possible to minimize the effect of voltage spikes on the driving circuit. While diodes protect electronics, they slightly slow the relay release time because the coil current decays more gradually through the diode.

### Benefits

Protects transistors, microcontrollers, and PLCs from high-voltage spikes. Prevents arcing across relay contacts, enhancing relay longevity. Reduces maintenance and replacement costs in systems with frequent relay switching.

In summary, diodes in relay protection circuits are essential for safely managing back EMF, ensuring the reliability and longevity of both the relay and the control electronics. Proper selection and installation of these diodes are critical for effective protection.

## Article Content

Do Relays Have Diodes? | Flyback Diodes Protect Relay

Yes, relays can have diodes. Specifically, many relays include a flyback diode, also known as a freewheeling diode, which is connected across the relay coil. The

Diodes inside relays

A diode can suppress that high voltage spike and protect any components around the relay. Also, depending on the diode, it can protect the relay from surges from electronics.

How Diodes Across Relay Coils Protect Circuits

You use a diode across relay coils to protect your electronic circuits from dangerous voltage spikes. When you energize the relay, the diode stays reverse-biased.

Protection Diode For Relay to Save Electronic Components

How does the Diode work in the relay circuit? The diode plays a crucial role in circuit protection and rectification. Its greatest characteristic is its one-way conductivity. That is the current

A Layman''s Guide to Coil Suppression

*© 2026 CJC FIBRE CONSULTANTS - All rights reserved*

For most relays and contactors, a common diode used is the well established 1N4007 type or something similar. Ideally this diode should be physically positioned as close to the relay coil as possible.

The Secret Behind That Diode Across a Relay

Want to See It in Action? Watch the video for a practical demonstration of what happens with and without the diode connected. You''ll see how the diode protects your circuit in real-time!

Flyback Diode Design Guide: Release Delay, PWM Recovery, EMI,

Engineering trade-offs of flyback diodes: relay release delay, reverse recovery losses in PWM, layout parasitics, and clamp strategies (Zener, TVS, RC snubber). Selection checklist and FAQ.

Modeling a Relay with Diode for Surge Protection

A relay with diode configuration provides transient voltage suppression when the relay is activated, which keeps the surge of current in the relay from burning out the switching circuitry.

Protecting Electronics with Relay Diodes

A relay diode protects circuits by safely dissipating the damaging voltage spike from a relay''s coil when it''s turned off, preventing component failure.

What is the optimal protection diode placement driving a relay

In any circuit where a transistor or FET is driving a DC relay, its common to see a reverse blocking diode added to suppress the inductive spikes, caused by fast current transitions (particularly t...

Do all relays need a diode in parallel with the coil?

I often see circuits with relays and diodes like this: Note the diode D1 in parallel with RLY1, at reverse polarity to the driving voltage V1. Per my research, the reason is that the relay coil is

Using diodes on a relay for spike protection

Hi folks. On the attached schematic, there''s a diode on the coil of the relay, to protect the system from the coil spike when the relay opens. Does it matter which way the 1N4004 diode is

Using Flyback Diodes in Relays Prevents Electrical Noise in Your ...

What is a flyback diode, and how does a flyback diode protect a circuit? When used properly, flyback diodes can reduce electrical noise and prevent flyback voltages from building up.

*© 2026 CJC FIBRE CONSULTANTS - All rights reserved*

Protection Diode For Relay to Save Electronic Components

Protect Electronics components by adding a Protection diode to your relay circuit. The theory explained here.

The Secret Behind That Diode Across a Relay

A diode across the coil safely absorbs that spike. So next time you use a relay in your project, don''t forget that tiny diode — it''s a small hero that protects your whole circuit!

Protecting a Relay Coil from a Surge

Just explained functions for protecting relays from surges. Hoping that you understood the case where a surge voltage is generated in a circuit with no protective circuit and where a surge

RELAY DRIVE PROTECTION

The relay contacts will remain closed for some time after the switch is opened due to the current stored in the relay coil. It would be desirable to speed up the current decay rate while retaining the

Component Options for Relay Coil Surge Suppression

Sections: Basics of Relay Coil Surge Suppression Using General Purpose Diodes Adding Zener Diodes Relays with Built-In Coil Surge Absorption Varistor and CR Circuits Summary Basics of

Related Video Reference

This video was associated with the source search result. Verify technical details against current product documentation and project requirements.

*© 2026 CJC FIBRE CONSULTANTS - All rights reserved*

## Contact Us

Continue your research online:

Website: https://cjcconsultants.co.za
Technical inquiry: https://cjcconsultants.co.za/contact.html

This document is for preliminary research. Verify specifications against current standards, product documentation and project requirements.

© 2026 CJC FIBRE CONSULTANTS - All rights reserved