Operational Amplifier Principle for Light-Controlled Lamps

Overview

This document details the design and implementation of a light-controlled lamp using an LM358 operational amplifier, BC337 transistor, and LDR sensor.

Key Takeaways

Operational amplifiers (op-amps) are commonly used in light-controlled lamp circuits to sense light levels via LDRs and switch lamps on or off automatically.

How Op-

Amps Work in Light-Controlled LampsIn light-controlled lamp circuits, an op-amp acts as a comparator. It compares the voltage from a light-dependent resistor (LDR) with a reference voltage set by a resistor network or potentiometer. The LDR's resistance changes with light intensity: high resistance in darkness and low resistance in bright light.

This voltage variation is fed into the op-amp's input terminals, and the op-amp output switches accordingly to control a transistor or relay that powers the lamp.

Typical Circuit Operation

Voltage Divider Setup: The LDR and a fixed resistor form a voltage divider. The voltage at the junction depends on ambient light.

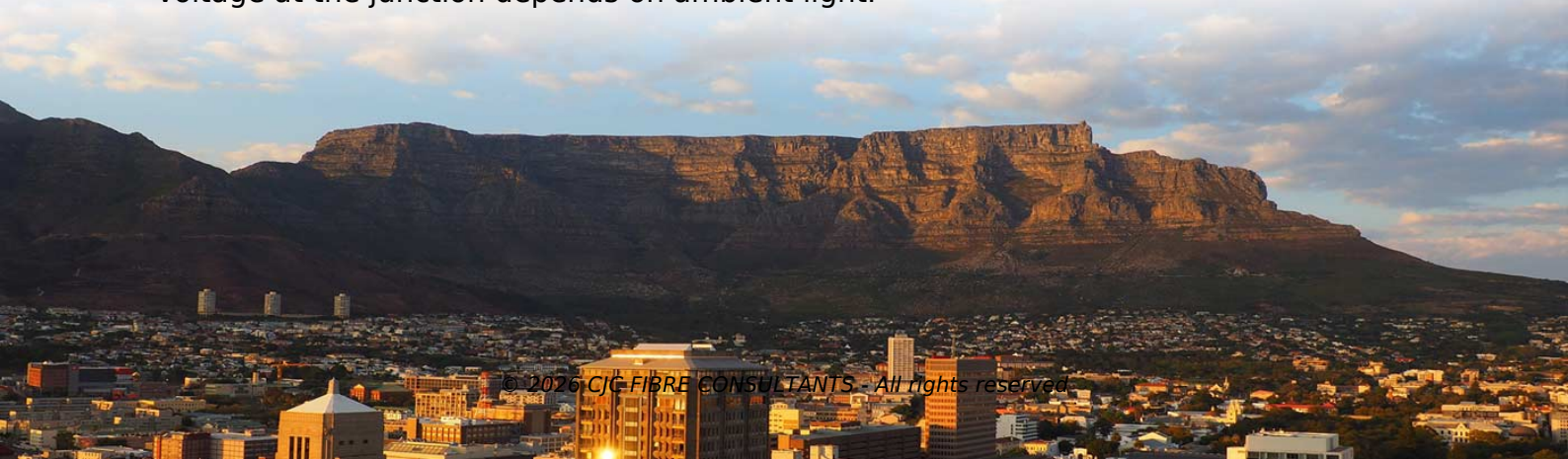

© 2026 CJC FIBRE CONSULTANTS - All rights reserved

Op-

Amp Comparator: The op-amp compares the LDR voltage to a reference voltage. If the light is below a threshold, the op-amp output goes high, turning on a transistor or relay to power the lamp. If the light exceeds the threshold, the op-amp output goes low, turning off the lamp.

Relay or Transistor Switching: The op-amp output drives a transistor or relay, which handles the higher current required by the lamp.

Key Op-

Amp Features for Light-Controlled LampsLow offset voltage and drift: Ensures accurate switching at the desired light level. Rail-to-rail input/output: Maximizes the usable voltage range, especially in low-voltage battery-operated circuits. Sufficient output current: Needed if the op-amp directly drives a transistor or relay.

High input impedance: Prevents loading the LDR voltage divider, maintaining sensitivity.

Common Op-

Amps UsedGeneral-purpose op-amps: LM358, TL072, or similar dual op-amps are widely used for simple light-activated switches. Precision op-amps: For more accurate threshold control, op-amps like OPA365 or TLV2372-Q1 are suitable due to low offset and rail-to-rail output.

Applications

Automatic room lighting that turns on at dusk and off at dawn. Street lamps and garden lights. Light-sensitive alarms or devices that respond to ambient light changes.

By using an op-amp in a light-controlled lamp circuit, designers can achieve reliable, adjustable, and energy-efficient automatic lighting that responds accurately to environmental light conditions.

© 2026 CJC FIBRE CONSULTANTS - All rights reserved

Article Content

Light-Controlled Lamp Design Guide | PDF | Operational Amplifier ...

This document details the design and implementation of a light-controlled lamp using an LM358 operational amplifier, BC337 transistor, and LDR sensor. It includes theoretical calculations, circuit

Light activated switch circuit with LDR and Op Amp

PDF file

exploring light sensitive circuits - RKessler

This paper shows you how you can build such a circuit with some simple electronic components and including an operational amplifier integrated circuit (IC). We will examine how the circuit works by

Light-Activated Switch Circuit Design | PDF

The document outlines the design of a light-activated switch circuit that turns on an LED when ambient light falls below a certain threshold using an LDR, an op-amp, and other components.

operational amplifier

The principle of the circuit seems straight forward- the voltage at the inverting input should be controlled by the current passing through the resistor, which in turn is the current passing

Automatic Night Lamp Circuit Diagram by LDR & LM358 OPAMP

This article explains an automatic night lamp circuit diagram using LDR and LM358 OPAMP which automatically turns the LEDs ON at night and OFF when it is daytime.

Automatic Op-amp night light circuit using IC-741

In this circuit, we use the LDR as a light receiver from sunlight. And, changing its resistance to be applied to other components in the circuit as we need. Read first for beginners: How

How to Build a Night Light Circuit Using an LM741

In this project, we will go over how to build an automatic night light circuit in which an LED will turn on automatically when it becomes dark using an LM741 op amp chip as a comparator.

Light-Sensitive Switch Circuit Using Op-Amp 741: A Comprehensive

© 2026 CJC FIBRE CONSULTANTS - All rights reserved

In this article, we will explore a simple, cost-effective, and user-friendly light-sensitive switch circuit utilizing the popular op-amp 741. This circuit operates based on light sensing,

Op amp or Operational Amplifier | Working Principle of Operational ...

Key learnings: Op Amp Definition: An op amp (operational amplifier) is defined as a DC-coupled voltage amplifier with a high voltage gain used in various electronic circuits. Working

Operational Amplifier Basics – Types and Characteristics in Detail -

Operational Amplifier Basics – Types and Characteristics in Detail - Operational amplifiers (op amps) are one of the most basic and most important components in the electronics products we use today. This

Operational Amplifiers: Chapters

An operational amplifier is a high-gain direct-coupled amplifier that is normally used in feedback connections. If the amplifier characteristics are satisfactory, the transfer function of the amplifier with

LDR/Light Dependent Resistor: Working Principle, Types and ...

We can use the light-dependent resistor circuit to control loads based on the intensity of light to overcome this problem. A device made of high-resistance semiconductor material is an LDR

OPERATIONAL AMPLIFIERS:

The Operational Amplifier (op amp) was invented in the 40''s. Bell Labs filed a patent in 1941 and many consider the first practical op amp to be the vacuum tube K2-W invented in 1952 by George Philbrick.

Operational Amplifiers Explained with Practical Circuits and Examples

Op Amp is a short name for operational amplifiers. It amplifies the difference between two input terminals and forces the output terminal to reflect the amplified voltage. It is called "operational" because it can

Op-Amp Basics: Introduction to the Operational Amplifier

Engineers currently have access to thousands of different op-amp ICs. It is somewhat misleading to identify all of these devices using the term “operational amplifier,” because in reality they form a diverse group of components. On the other hand, op-amps consistently exhibit various

Operational Amplifiers

© 2026 CJC FIBRE CONSULTANTS - All rights reserved

Introduction The operational amplifier (op-amp) is a voltage controlled voltage source with very high gain. It is a five terminal four port active element. The symbol of the op-amp with the associated

Operational Amplifiers Basics, Characteristics, Types and ...

Operational amplifiers, working and applications as amplifier, follower, comparator, along with 3 requirements. Also find an application- audio preamplifier

Operational Amplifier (Op Amp): Basics, Operation,

The article provides an overview of operational amplifier (op-amp), discussing their basic structure, internal operation, and various types of control

Related Video Reference

This video was associated with the source search result. Verify technical details against current product documentation and project requirements.

Contact Us

Continue your research online:

Website: https://cjcconsultants.co.za
Technical inquiry: https://cjcconsultants.co.za/contact.html

This document is for preliminary research. Verify specifications against current standards, product documentation and project requirements.

© 2026 CJC FIBRE CONSULTANTS - All rights reserved